

Section 3.2. XOR operation

EEEC382


minterm and maxterm

1

- XOR (\oplus)
 - Exclusive-OR
 - Some interpretations:
 - X not equal to Y
 - X and Y has odd number of 1's

X	Y	$X \oplus Y$
0	0	0
0	1	1
1	0	1
1	1	0

$$X \oplus Y = X'Y + XY'$$

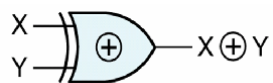

EEEC382

minterm and maxterm

2

- Theorems:

- $X \oplus 0 = X$

- $X \oplus 1 = X'$

- $X \oplus X = 0$

- $X \oplus X' = 1$

- $X \oplus Y = Y \oplus X$

- $(X \oplus Y) \oplus Z = X \oplus (Y \oplus Z) = X \oplus Y \oplus Z$

- $X(Y \oplus Z) = XY \oplus XZ$

- $(X \oplus Y)' = X \oplus Y' = X' \oplus Y = XY + X'Y'$

- XNOR (Ξ)

- Inverted exclusive-OR

- Ξ notation not used in other text


- Some interpretations:

- X equal to Y (i.e., equivalence operator)

- X and Y has even number of 1's

X	Y	$(X \oplus Y)'$
0	0	1
0	1	0
1	0	0
1	1	1

$$(X \oplus Y)' = X'Y' + XY$$

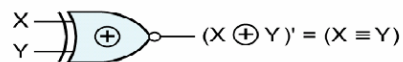

- Equivalence is the complement of XOR:

$$\begin{aligned}(X \oplus Y)' &= (X'Y + XY')' \\ &= (X + Y')(X' + Y) \\ &= X(X' + Y) + Y'(X' + Y) \\ &= XX' + XY + Y'X' + Y'Y \\ &= XY + X'Y' \\ &= (X \equiv Y)\end{aligned}$$

Assignment

- Read Section 3.2
- Problems:
3.8, 3.9, 3.10

Chap 4. Minterm and Maxterm Expansions

EEEC382

minterm and maxterm

7

Outline

- Conversion of English Sentence to Boolean Equations
- Combinational Logic Design Using a Truth Table
- Minterm and Maxterm Expansions
- Incompletely Specified Functions
- Examples of Truth Table Construction

EEEC382

minterm and maxterm

8


Conversion of English Sentence to Boolean Equations

- Mary watches TV if it is Monday night and she has finished her homework
F A B

$$F = A B$$

- The alarm will ring iff the alarm switch is on and the door is not closed
Z A B'
or it is after 6pm and the window is not closed
C D'

$$Z = AB' + CD'$$

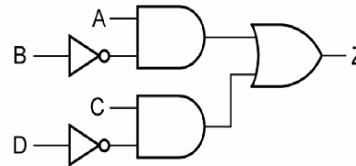

EEC382

minterm and maxterm

9

- Consider A, B, C are three votes, which can be yes (1) or no (0). An output U is 1 iff the vote is unanimous
 - U is 1 iff ABC are all 1's or all 0's
 - $U = ABC + A'B'C'$
- An output M is 1 iff there is a majority vote
 - $M = ?$
 - Somewhat tedious (and error-prone) to derive the logic expression
 - Truth table is a systematic way to derive the expression


EEC382

minterm and maxterm

10

Combinational Logic Design Using a Truth Table

- Switching circuit Logic design using truth table



A	B	C	f	f'
0	0	0	0	1
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	1	0
1	0	1	1	0
1	1	0	1	0
1	1	1	1	0

EEC382

minterm and maxterm

11

- f is 1 if (row 3 is 1) or (row 4 is 1) or (row 5 is 1) or (row 6 is 1) or (row 7 is 1)
- Logic expression for
 - (row 3 is 1): $A'BC$
 - (row 4 is 1): $AB'C'$
 - (row 5 is 1): $AB'C$
 - (row 6 is 1): ABC'
 - (row 7 is 1): ABC
- Derive algebraic expression for $f = 1$


$$f = A'BC + AB'C' + AB'C + ABC' + ABC$$

- f can simplified

$$f = A'BC + AB' + AB$$

$$= A'BC + A \quad \text{by Thm 8D: } x+yz=(x+y)(x+z)$$

$$= A + BC$$

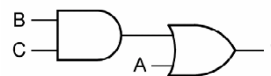

EEC382

minterm and maxterm

12

- It is easier to think in term of SOP
- It is less intuitive to derive POS expression directly
- Alternative way to construct POS expression
 - Find SOP expression for f'
 - Invert f' to get f

- $f' = A'B'C' + A'B'C + A'BC'$

- $f = (f)'$

$$= (A'B'C' + A'B'C + A'BC)'$$

$$= (A + B + C)(A + B + C')(A + B' + C)$$
- f can be simplified

$$= (A + B)(A + B' + C)$$

$$= A + B(B' + C)$$

$$= A + BC$$

A	B	C	f	f'
0	0	0	0	1
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	1	0
1	0	1	1	0
1	1	0	1	0
1	1	1	1	0

- An different interpretation (less intuitive):
 - f is 0 if one of the first three rows is 0
 - Row 0 is 0: $A=B=C=0$; i.e., $A + B + C$ is 0
 - Row 1 is 0: $A=B=0 C=1$; i.e., $A + B + C'$ is 0
 - Row 2 is 0: $A=C=0 B=1$; i.e., $A + B' + C$ is 0

- f is 0 if one of the first three rows is 0

$$f = (A + B + C)(A + B + C')(A + B' + C)$$

A	B	C	f	f'
0	0	0	0	1
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	1	0
1	0	1	1	0
1	1	0	1	0
1	1	1	1	0

Minterm and Maxterm Expansions

- A minterm of n variables is a product of n literals in which each variable appears exactly once in true or complemented form, but not in both.
- Sum of minterms is referred to as a minterm expansion or a standard SOP.
- Minterm is written in abbreviated form as m_i where i is the row whose values make $m_i=1$
- The row is represented as a binary number

3-variable truth table

- Note that the order of variables is important i.e., the row is (A B C) not (A C B), (C A B) etc.

Row No.	A B C	Minterms	Maxterms
0	0 0 0	$A'B'C' = m_0$	$A + B + C = M_0$
1	0 0 1	$A'B'C = m_1$	$A + B + C' = M_1$
2	0 1 0	$A'BC' = m_2$	$A + B' + C = M_2$
3	0 1 1	$A'BC = m_3$	$A + B' + C' = M_3$
4	1 0 0	$AB'C' = m_4$	$A' + B + C = M_4$
5	1 0 1	$AB'C = m_5$	$A' + B + C' = M_5$
6	1 1 0	$ABC' = m_6$	$A' + B' + C = M_6$
7	1 1 1	$ABC = m_7$	$A' + B' + C' = M_7$

- f represented in sum-of-minterms format:
 $f(A, B, C) = m_3 + m_4 + m_5 + m_6 + m_7$
 $= \Sigma m(3, 4, 5, 6, 7)$
- Again, argument order (A,B,C) is important

A	B	C	f	f'
0	0	0	0	1
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	1	0
1	0	1	1	0
1	1	0	1	0
1	1	1	1	0

Row No.	A	B	C	Minterms	Maxterms
0	0	0	0	$A'B'C' = m_0$	$A + B + C = M_0$
1	0	0	1	$A'B'C = m_1$	$A + B + C' = M_1$
2	0	1	0	$A'BC' = m_2$	$A + B' + C = M_2$
3	0	1	1	$A'BC = m_3$	$A + B' + C' = M_3$
4	1	0	0	$AB'C' = m_4$	$A' + B + C = M_4$
5	1	0	1	$AB'C = m_5$	$A' + B + C' = M_5$
6	1	1	0	$ABC' = m_6$	$A' + B' + C = M_6$
7	1	1	1	$ABC = m_7$	$A' + B' + C' = M_7$

- Finding sum-of-minterms for a logic expression

- Truth table
- Algebraic derivation

- E.g.,

$$f(a,b,c,d) = a'(b' + d) + acd'$$

$$f = a'b' + a'd + acd'$$

$$= a'b'(c + c')(d + d') + a'd(b + b')(c + c') + acd'(b + b')$$

$$= a'b'c'd' + a'b'c'd + a'b'cd' + a'b'cd + a'b'c'd + a'b'cd$$

$$+ a'bc'd + a'bcd + abcd' + ab'cd'$$

$$= a'b'c'd' + a'b'c'd + a'b'cd' + a'b'cd + a'bc'd + a'bcd$$

$$+ abcd' + ab'cd'$$

Maxterm

- A maxterm of n variables is the sum of n literals in which each variable appears exactly once in true or complemented form, but not in both.
- product of maxterms is referred to as a maxterm expansion or a standard POS.
- Maxterm is written in abbreviated form as M_i where i is the row whose values make $M_i = 0$;
- Relationship between m_i and M_i
 $(m_i)' = M_i$ $m_i = (M_i)'$

- f represented in product-of-maxterms format:
 $f(A, B, C) = M_0 M_1 M_2$
 $= \prod M(0, 1, 2)$
- Argument order (A,B,C) is important

A	B	C	f	f'
0	0	0	0	1
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	1	0
1	0	1	1	0
1	1	0	1	0
1	1	1	1	0

Row No.	A B C	Minterms	Maxterms
0	0 0 0	$A'B'C' = m_0$	$A + B + C = M_0$
1	0 0 1	$A'B'C = m_1$	$A + B + C' = M_1$
2	0 1 0	$A'BC' = m_2$	$A + B' + C = M_2$
3	0 1 1	$A'BC = m_3$	$A + B' + C' = M_3$
4	1 0 0	$AB'C' = m_4$	$A' + B + C = M_4$
5	1 0 1	$AB'C = m_5$	$A' + B + C' = M_5$
6	1 1 0	$ABC' = m_6$	$A' + B' + C = M_6$
7	1 1 1	$ABC = m_7$	$A' + B' + C' = M_7$

Sum-of-minterms and Product-of-maxterms conversion

- Procedure
 - Given: function f in sum-of-minterms format
 - Write f' in sum-of-minterms format
Note that f' consists of all minterms not in f
 - Find (f') , which is in product-of-maxterms format
Note that $f = (f)'$


- E.g.,
 $f(A, B, C) = m_3 + m_4 + m_5 + m_6 + m_7$
 $f'(A, B, C) = m_0 + m_1 + m_2$
 $f = (f)' = M_0 M_1 M_2$

A	B	C	f	f'
0	0	0	0	1
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	1	0
1	0	1	1	0
1	1	0	1	0
1	1	1	1	0

Incompletely Specified Functions

- Some input combinations of function may not be used or possible
- e.g., F and B are two signals control a model car to drive forward or backward. An function M is 1 if car in motion and 0 if car is still. The input combination "11" is not possible.
- The condition is known as don't care (denoted **d** in truth table).
- When the function is implemented, either 0 or 1 can be assigned
- Good assignment can simplified the final circuit

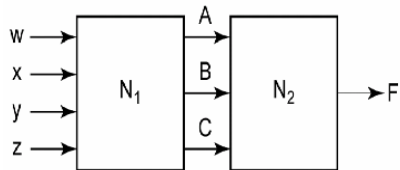- E.g.,
A large digital system would be divided into many subsystems, i.e., N_1 and N_2 as an example.
- Assume N_1 does not generate all possible combinations of values for A, B, C (e.g., 001, 110).
- $F = \sum m(0, 3, 7) + \sum d(1, 6)$
- $F = \prod M(2, 4, 5) \cdot \prod D(1, 6)$



A	B	C	F
0	0	0	1
0	0	1	X
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	0
1	1	0	X
1	1	1	1

- Alternatives:
 1. Assume $d = 0$ for both X's:
 $F = A'B'C' + A'BC + ABC = A'B'C' + BC$
 2. Assume $d = 1$ to the first X and $d = 0$ for the 2nd X:
 $F = A'B'C' + A'B'C + A'BC + ABC = A'B' + BC$
 3. Assume $d = 1$ to both X's:
 $F = A'B'C' + A'B'C + A'BC + ABC' + ABC$
 $= A'B' + BC + AB$
- Choice 2 leads to the simplest solution


Examples of Truth Table Construction

- Design simple binary adder that adds two 1-bit binary numbers (a, b) and produces 2-bit sum.

- $X = AB$
- $Y = A'B + AB'$

A	B	SUM	
		X	Y
0	0	0	0
0	1	0	1
1	0	0	1
1	1	1	0

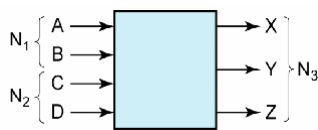- Design simple binary adder that adds two 2-bit binary numbers (N_1, N_2) and produces 3-bit sum (N_3).



TRUTH TABLE:			TRUTH TABLE:		
N_1	N_2	N_3	N_1	N_2	N_3
$\overline{A} B$	$\overline{C} D$	$\overline{X} Y Z$	$\overline{A} B$	$\overline{C} D$	$\overline{X} Y Z$
0 0	0 0	0 0 0	1 0	0 0	0 1 0
0 0	0 1	0 0 1	1 0	0 1	0 1 1
0 0	1 0	0 1 0	1 0	1 0	1 0 0
0 0	1 1	0 1 1	1 0	1 1	1 0 1
0 1	0 0	0 0 1	1 1	0 0	0 1 1
0 1	0 1	0 1 0	1 1	0 1	1 0 0
0 1	1 0	0 1 1	1 1	1 0	1 0 1
0 1	1 1	1 0 0	1 1	1 1	1 1 0

- $X(A,B,C,D) = \Sigma m(7, 10, 11, 13, 14, 15)$
- $Y(A,B,C,D) = \Sigma m(2, 3, 5, 6, 8, 9, 12, 15)$
- $Z(A,B,C,D) = \Sigma m(1, 3, 4, 6, 9, 11, 12, 14)$

Assignment

- Read Sections 4.1, 4.2, 4.3, 4.5, 4.6
- Section 4.7 to be covered later
- Problems:
4.2, 4.3, 4.7, 4.9, 4.13, 4.16, 4.21, 4.23, 4.24